

## CONTENTS

1	Terminology
2	Parameters
3	Other parameters
4	Inductor types
5	Advantages of passive networks
6	Inductors in passive filters
7	Inductors in switched mode power supplies (SMPS)
8	Basic topography
9	Inductor selection
10	Design example
11	Modelling inductors in SPICE
12	Design example
13	Limitations
14	Summary
15	EMC design considerations

## 1. TERMINOLOGY

Reading a specification for an inductor is considered a simple task, however, there is often some confusion even over the meaning of relatively straight forward parameters. The following list is intended to give a basic understanding of what parameters are stated by C&D Technologies (NCL).

## 2. PARAMETERS

### INDUCTANCE (L):

The classical definition of inductance is a constant that relates the magnetic flux linking a circuit to the current flowing in the circuit. The inductance is measured as a reactance to an AC signal at a single frequency (typically 10mV at 1kHz).

### MAXIMUM DC CURRENT ( $I_{DC}$ ):

The maximum DC current is defined as the DC current at which the inductance falls to 90% of its nominal value (see figure 1). However, this does not recognise the effect of self heating also contributing to a change in inductance (usually inductance falls as the temperature rises). Consequently the maximum DC current is limited to a temperature rise of 30°C. Therefore the maximum DC current is the value at which the inductance falls to 90% of its nominal value or until its temperature rise reaches 30°C, whichever is sooner. *When making comparisons with Inductors it is worth noting that many manufacturers quote a 30% drop which gives the impression of a higher current rating. C&D Technologies (NCL) Inductors will withstand current spikes greater than IDC for short periods.*


### SELF RESONANT FREQUENCY ( $f_0$ ):

Self resonance occurs when the impedance of the inductor is purely resistive. At this frequency the capacitive effect of the wire and the inductance cancel and the relative signal phase across the inductor is zero.

### QUALITY FACTOR (Q):

In single reactive components the quality factor is usually the ratio of the reactance and resistance (ideally  $Q = L/R_{DC}$ , where  $R = 2 f$ ). The value quoted in the specification is a measured value at a specific frequency, this compensates for the capacitance of the wire (all measurements are made on a HP4191A and HP4192A impedance analyser with a 10mV signal).

Figure 1: Maximum DC Current

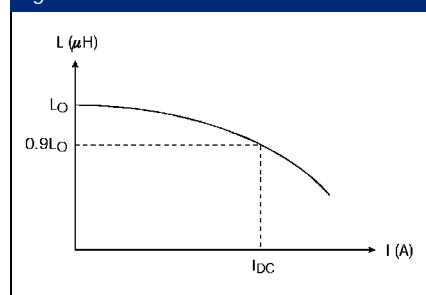

### INDUCTANCE TEMPERATURE COEFFICIENT:

The change in inductance per unit temperature change. Measured under zero bias conditions and expressed in parts per million (ppm).

### RESISTANCE TEMPERATURE COEFFICIENT:

The change in DC wire resistance per unit temperature change. Measured under low DC bias (<1VDC) and expressed in parts per million (ppm).

### CURRIE TEMPERATURE ( $T_C$ ):

The temperature beyond which the core material loses its magnetic properties.

### MAGNETIC SATURATION FLUX DENSITY ( $B_{SAT}$ )

A core parameter which indicates the maximum flux the material can be induced to hold. At this value of flux density all magnetic domains within the core are magnetised and aligned.

## 3. OTHER PARAMETERS

### SATURATION:

Saturation of an inductor occurs when the core can no longer store magnetic energy, (energy storage =  $\frac{1}{2} LI^2$ ).

### EMI:

Electromagnetic interference in inductors refers to the amount of magnetic field radiated away from the inductor itself, that is into "space". This field may cause interference with other magnetically sensitive components and requires consideration in circuit design and layout and may determine the selection of inductive components in certain applications.

## 4. INDUCTOR TYPES

### BOBBIN

#### (1400, 1700, 1800R, SERIES)

This inductor core shape usually supports very low losses, hence high efficiency designs, that can often be wound to permit high current at relatively high inductance values. Bobbins do exhibit higher EMI than toroids or pot cores, however, they are usually lower cost than pot cores, more compact and exhibit higher saturation current than toroidal inductors of comparable physical size.

Suitable for high current designs, such as switching regulators and compact high current filtering, where core saturation is to be avoided.

### TOROID


Toroidal inductors exhibit very low EMI, the shape of the core means the magnetic path flows only within the inductor and hence stray field is virtually eliminated. At high inductance values saturation can occur at relatively low current.

The most common form used in switching

# INDUCTORS

## Application Notes

Figure 2: Simple Filter Construction

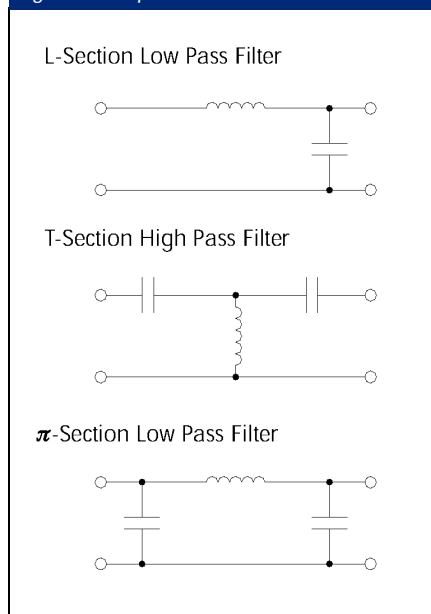

regulators due to their EMI properties, toroid inductors are also useful in applications where saturation can be used as either a limiting or feedback mechanism (e.g. chokes, power filters). Toroids can be used at up to several MHz with careful choice of core material.

### 5. ADVANTAGES OF PASSIVE NETWORKS

It is easy in the "silicon age" to dismiss inductors as circuit elements in favour of what are considered cheaper, physically smaller

and lighter active networks. However, there are many properties of inductors which cannot be produced using "cheap" silicon, one that is immediately brought to mind is use in power circuitry. Another area in which an inductor may prove to be cheaper is in a simple filter circuit, active filters are usually considerably more complex and often relatively expensive to implement as simple low order filters compared to passive inductive designs.

At high frequencies, silicon and RC networks become limited, stray capacitance and transistor switching frequencies can restrict design capability and increase cost, amplifier stability can also cause serious problems and grounding configurations require special attention. While not alleviating all the problems associated with high frequency design, low DC resistance of inductors are easily characterised and predictable frequency responses can make circuit design and analysis of circuit behaviour easier.

There are certainly some definite advantages in using inductors in modern circuit designs and these passive elements should not be neglected. The following design notes give some basic ideas for use of C&D Technologies (NCL) range of inductors. The designs can be used as shown or alternatively the basic ideas adapted to the readers own requirement. The notes are not exhaustive and we welcome feedback and application ideas from any customers, similarly we are always willing to discuss your requirement and can, if required, custom design an inductor for your application.

Figure 3: Basic Boost Converter

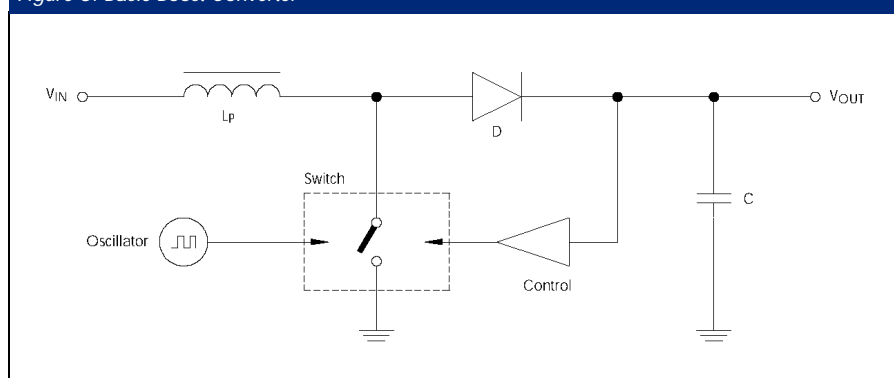


Table 3: Inductor Selection For MAX631 IC

INDUCTOR PART NUMBER	INDUCTANCE ( $\mu$ H)	START-UP VOLTAGE (V)	OUTPUT CURRENT (mA)	EFFICIENCY (%)
18R224	220	3.0	50	75
18R224	220	3.4	100	67
18R334	330	3.0	50	75
18R334	330	3.4	100	67
18R474	470	3.0	50	76
18R474	470	3.6	100	66

## 6. INDUCTORS IN PASSIVE FILTERS

### SIMPLE FILTERS

Simple filters can be easily constructed with inductor and capacitor elements. These filters have the advantage of being easy to calculate and characterise the frequency response. They exhibit few of the secondary effects and stability problems associated with their active counterparts. In power line filtering, inductors and relatively small capacitors can be used to produce a smoothed ripple from a spiked input response, ideal for reducing noise in switching regulator circuits and power lines in noisy environments.

Simple L, T and  $\pi$  section filters can be constructed to provide low, high and band pass functions (see figure 2). There are many texts on this subject and these should be consulted for details on more complex filters and interaction between sections. These pages are simply illustrative of applications for C&D Technologies (NCL) inductor parts.

## 7. INDUCTORS IN SWITCHED MODE POWER SUPPLIES (SMPS)

There are many silicon switching circuits available on the market from most analog silicon vendors (Maxim, Linear Technology, Motorola etc.). All the design notes which accompany these devices recognise the importance of correct inductor selection to achieve the optimum performance of the SMPS design. Refer to separate data sheet, Silicon Support Magnetics.

## 8. BASIC TOPOGRAPHY

The majority of switching regulator ICs operate a "pulse skipping" method of regulation. This employs a free running oscillator and a switch to control the oscillator as a driver for an internal or external power switch. The circuit is controlled by a feedback comparator, the switch driving the output when the circuit falls below the desired output level and remaining off once the level is exceeded (see figure 3).

There are many configurations for using inductors and transformers in this type of SMPS, however, here the boost regulator will only be considered for our example.

## 9. INDUCTOR SELECTION

The inductance value for a switching regulator must be high enough to prevent excessive current through the diode and low enough to store sufficient energy in the core. The DC resistance should be low to reduce losses and prevent self heating. The core must also be capable of storing the required energy without saturating. For general purpose use bobbin wound inductors are excellent for most cases, however, in EMI

sensitive applications a toroid may be preferable.

The peak current ( $I_{PK}$ ) and inductance ( $L_P$ ) value should be calculated for two worst case conditions (i.e. maximum and minimum values of  $I_{PK}$  and  $L_P$ ). The final choice should be an inductor whose inductance is in between the limits of the calculated values and which has a DC current rating in excess of the maximum peak current calculated.

$$(1) I_{PK} = \frac{4 I_{OUT} (V_{OUT} - V_D)}{(V_{IN} - V_{SW} - V_D)}$$

$$(2) L_P = \frac{t_{ON} (V_{IN} - V_{SW} - V_{OUT})}{I_{PK}}$$

Where  $V_{OUT}$  is the required output voltage,  $V_{IN}$  is the input supply voltage,  $I_{OUT}$  is the required output current (load current),  $V_{SW}$  is the voltage drop across the switching element and  $V_D$  is the voltage drop in the diode.

## 10. DESIGN EXAMPLE:

### 500MW SMPS USING MAX631 AND 1800R SERIES INDUCTORS

The MAX631 is one of the simplest switching regulator ICs to use as this contains all circuit functions except for the output capacitor and boost inductor (figure 5). The circuit is a 5V step-up boost regulator with a wide input range from the start-up voltage to around 4.5V. The performance quoted in table 3 was achieved using radial leaded inductors and a standard DIL IC.

Note: The quoted maximum power rating of many IC switching regulators are only applicable at high output voltage (i.e. low peak current). Consequently if trying to produce power at low output voltage (i.e. less than 12V), use a higher power rated switching circuit or external switching

Figure 5: MAX631 and 1800R Series


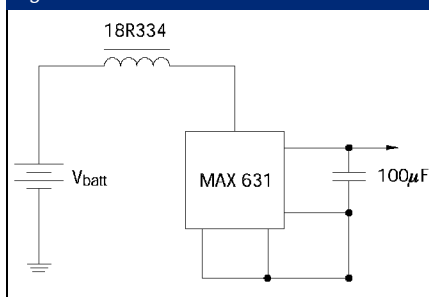


Figure 6: Equivalent Inductor Circuit

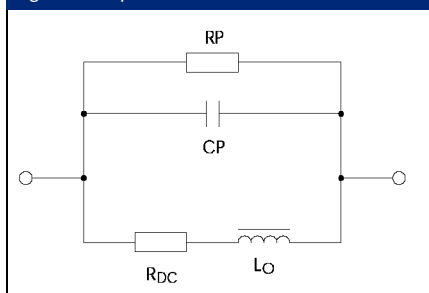

transistor.

## 11. MODELLING INDUCTORS IN SPICE

If a SPICE simulation of an inductor is required the simple standard value may not be adequate for all occasions, particularly in situations where the inductor is being used either near its maximum DC current value or when operated at near resonant frequency. In a circuit using many low resistance parts or where low resistance is significant, the effect of the DC resistance of the inductor may be noticeable in the circuit, especially when using high value inductors that have high DC resistance. The specification for an inductor gives sufficient data to accurately model some of the more complex effects of an inductor in a circuit.

An inductor model can be constructed from

4 passive elements, an ideal series inductor and resistor, a parallel capacitor and parallel resistor (see figure 6). The value of the series resistor is defined by the DC resistance value in the device specification (e.g. for a 1900 series 100µH inductor,  $R_{DC}=0.065 \Omega$ ). The value of the parallel capacitor can be derived from the self resonant frequency ( $f_0$ ) of the part, since this is the point at which the reactance of the inductor is zero (i.e. the impedance is purely resistive). At self resonance the capacitance is given by;

$$(3) C_P = \frac{1}{(2 f_0)^2 L_O}$$

Magnetic core loss is modelled as a parallel resistor ( $R_P$ ) across the terminals. The value can be calculated from the quality factor ( $Q$ );

$$(4) R_P = Q (2 f_0) L_O$$

This parallel resistor limits the simulated self resonance rising to 'infinity'. The model with

Figure 7 : 18R 334 Impedance Simulation


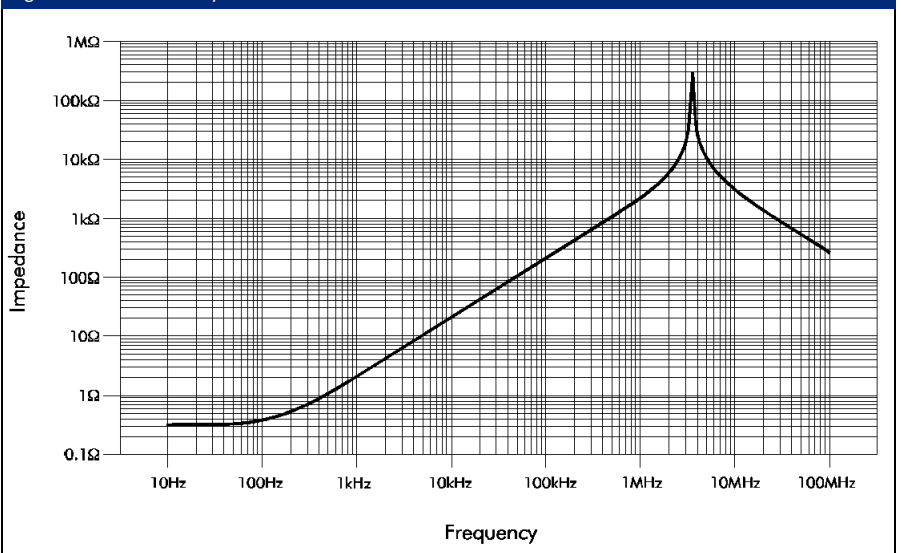


Figure 7 : 18R 334 Impedance Simulation

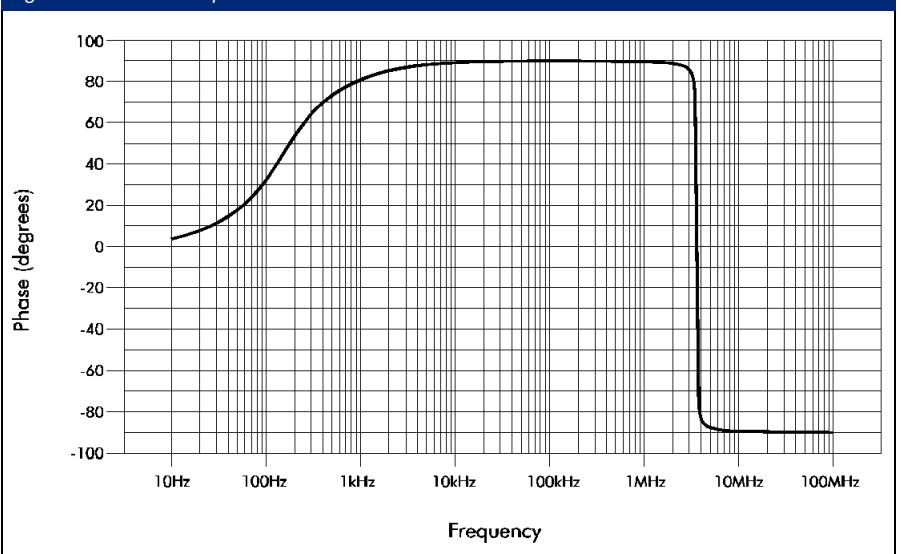

# INDUCTORS

## Application Notes

these four basic circuit elements models the inductors impedance and phase behaviour over a wide frequency range (see figures 7 and 8).

The inductance value is not constant as the DC current through the device reduces its inductance, since part of the core is magnetised (figure 1). The standard inductor model in version 2G6 of SPICE can accommodate this effect as a polynomial expression for the inductance as a function of current (equation 5), this can be entered in the standard inductor description in SPICE.

$$(5) L_l = L_0 + L_1 I + L_2 I^2 + \dots + L_n I^n$$

Where  $n \geq 20$ .

A simple 2nd order polynomial is sufficient to model this effect and the maximum DC current value can be used to determine the coefficient,  $L_2$ . If the inductance is 90% of its nominal value,  $L_0$ , at the maximum DC current,  $I_{DC}$ , then the polynomial equation is;

$$(6) 0.9 L_0 = L_0 + L_2 I_{DC}^2$$

Hence the coefficient is given by;

$$(7) L_2 = - \frac{0.1 L_0}{I_{DC}^2}$$

An accurate and relatively complex model for an inductor can now be constructed using data sheet values only, hence no additional measurements by the user are required.

### 12. DESIGN EXAMPLE:

#### SPICE 2G6 EXAMPLE

The following example is a model for a 1800R series 330µH inductor (18R 334) where  $L_0=330\mu\text{H}$ ,  $R_{DC}=0.315$ ,  $I_{DC}=0.73\text{A}$ ,  $Q=49$  and  $f_0=3.57\text{MHz}$ .

```
.SUBCKT L18R334 1 2
```

```
LO 3 2 POLY 330E - 6 0 - 6.19E - 5
```

```
RDC 1 3 0.315
```

```
CP 1 2 6.02E - 12
```

```
RP 1 2 363K
```

```
.ENDS L18R334
```

### 13. LIMITATIONS

The above model is now quite sophisticated for an inductive element, however, there are still limitations and this should be borne in mind. The model assumes that there is no variance of resistance and capacitance with DC current, at low values of these parameters this may be adequate as these will tend to be swamped by the rest of the circuit. The major limitation is in the lack of temperature modelling of the inductor, however, this is a general limitation of SPICE. Some temperature modelling for the resistor could be incorporated, however, the heating effect of the power dissipated in the inductor ( $I^2R$  term) is not modelled.

### 14. SUMMARY

It is possible to simulate several complex aspects of inductor operation using only 3 additional passive elements and a simple polynomial expression. The resulting model gives accurate inductor simulations in SPICE over a wide range of operating conditions with a minimal increase in computation time (only one extra node is introduced).

### 15. EMC DESIGN CONSIDERATIONS

The imminent EC regulations regarding electromagnetic compatibility (EMC) will effect many aspects of circuit and system design.

However, there are many considerations that can be applied generally to reduce both the emissions from and susceptibility to electromagnetic interference (EMI).

There are many areas where the use of inductors in decoupling and filtering applications will help. However, there may also be situations where the inductive element in a switching circuit is the major cause of EMI. As a manufacturer C&D Technologies (NCL) is committed to minimising emissions from its own components and to helping its customers achieve EMC compatibility by

correct component choice and design, to this end we have compiled the following list of general design considerations.

- Reduce high frequency (particularly radio frequency) loops in supply lines.
- De-couple supply lines at local boundaries (use RCL filters with  $Q \geq 2$ ).
- Use low pass filters on signal lines to reduce band width to signal minimum.
- Keep return and feed loops close on wide band width signal lines.
- Terminate lines carrying HF or RF signals correctly (this minimises reflection, ringing and overshoot).
- Avoid slit apertures in pcb layout, particularly in ground planes or near current paths.
- Use common mode chokes between current carrying and signal lines to increase coupling and cancel stray fields.
- Use discrete components and filters where possible.
- Ensure filtering of cables and over voltage protection (this is especially true of cabling that is external to the system, if possible all external cabling should be isolated at the equipment boundary).
- Isolate individual systems where possible (especially analogue and digital systems, on both power supply and signal lines).
- If available, use shielding on fast switching circuits, mains power supply components and low power circuitry.

In general, keeping the band width of all parts of the system to a minimum and isolating circuits where possible reduces susceptibility and emissions.

C&D Technologies (NCL) Limited reserve the right to alter or improve the specification, internal design or manufacturing process at any time, without notice. Please check with your supplier or visit our web site to ensure that you have the current and complete specification for your product before use.

© C&D Technologies (NCL) Limited 2000

AN007.1

No part of this publication may be copied, transmitted or stored in a retrieval system or reproduced in any way including, but not limited to, photography, photocopy, magnetic or other recording means, without written permission from C&D Technologies (NCL) Limited.

Instructions for use are available from [www.dc-dc.com](http://www.dc-dc.com)

**C&D Technologies (NCL) Ltd**  
Tanners Drive, Blakelands North  
Milton Keynes MK14 5BU, England  
Tel: +44 (0)1908 615232  
Fax: +44 (0)1908 617545  
email: [info@cdtechno-ncl.com](mailto:info@cdtechno-ncl.com)

**www: <http://www.dc-dc.com>**

**C&D Technologies (NCL), Inc.**  
8917 Glenwood Avenue, Raleigh  
NC 27612, USA  
Tel: +1 (919) 571-9405  
Fax: +1 (919) 571-9262  
email: [info@us.cdtechno-ncl.com](mailto:info@us.cdtechno-ncl.com)

 **TECHNOLOGIES**  
Power Solutions